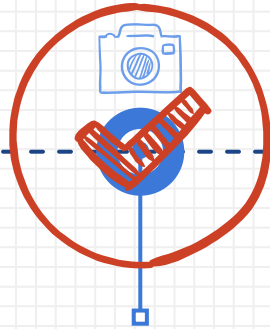


EECS16A Touchscreen 1





Semester Outline



Imaging
Module



Touchscreen
Module




APS
Module

- Breadboarding
- Build multiple functional circuits
- Learn how to use Multimeter




Breadboarding basics

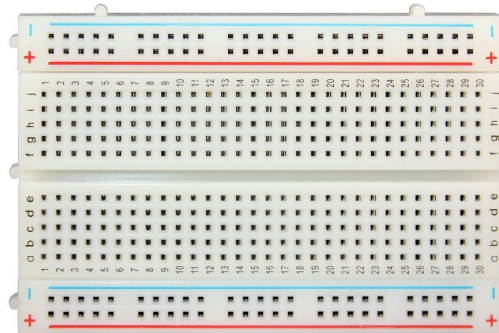- Similar to Imaging 1: Intro to Breadboarding
- Build up breadboarding skills
 - Connect to concepts in lecture, including Voltage Dividers and KVL
- Very important skill: prototype, debug, and translate theoretical ideas into real circuits




Tinkercad

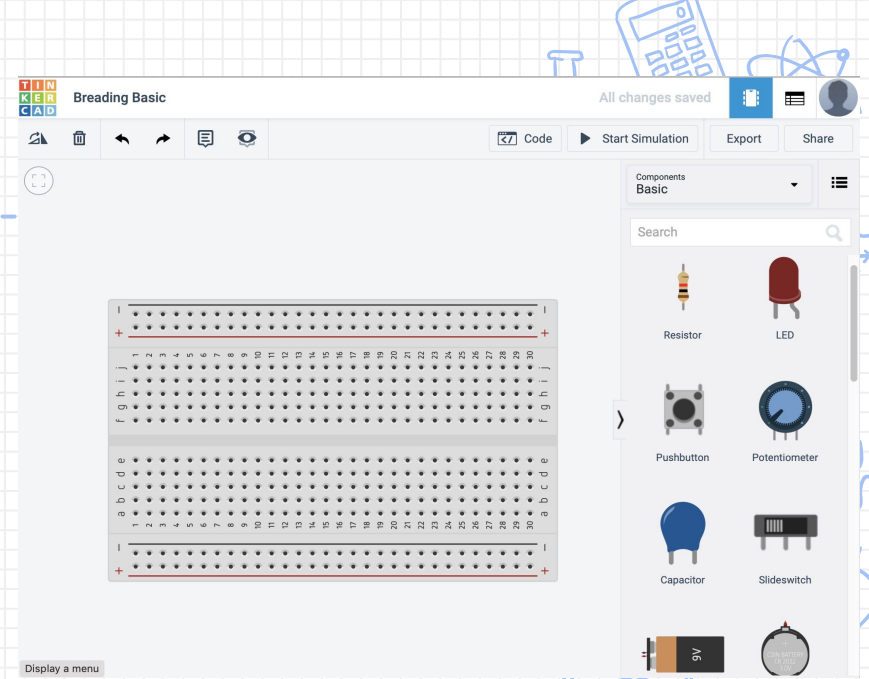- Circuit design prototyping software
 - Primary circuit software in this course
 - Useful for many different electrical projects
- Ran online using an Autodesk account




Launchpad Review

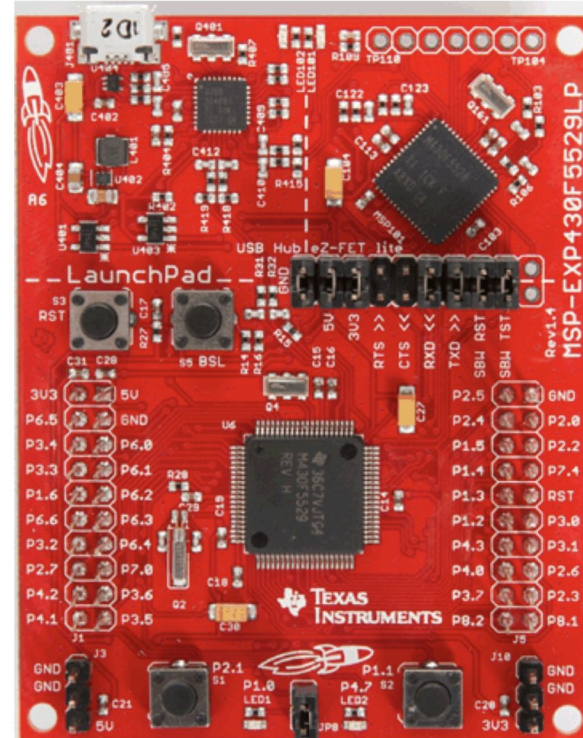
- Micro-Controller
- Power Supply
- Voltmeter



Multimeter (Circuit Debugger)

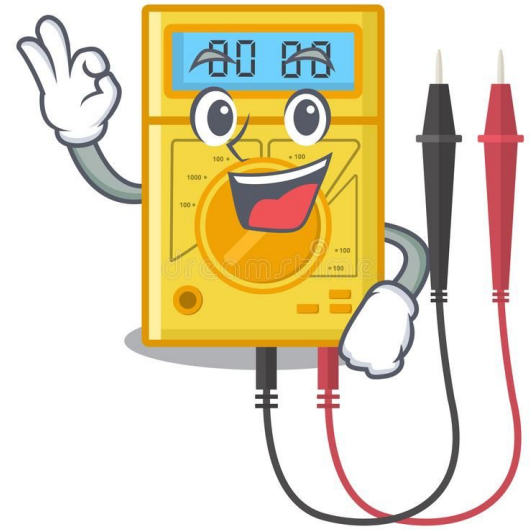- Voltmeter
 - Infinite resistance
 - Connect in parallel with component
- Ammeter
 - Very low resistance
 - Act as a wire in the circuit
 - Connect in series with component
- Ohmmeter
 - Remove resistor from circuit before use
 - Connect in parallel with resistor






diode




diode



current

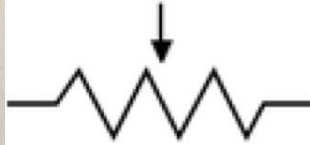



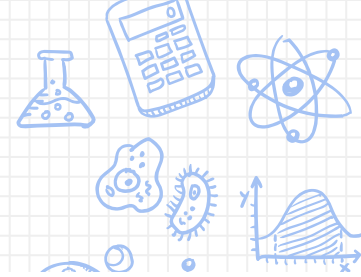

Voltage Divider Circuit

What is the voltage value u_2 at Node 2?


$$I_y = I_z = V_s / (R_1 + R_2) \text{ (Ohm's Law)}$$


$$u_2 - u_0 = R_2 * I_z$$

$$u_2 - 0 = R_2 * V_s / (R_1 + R_2)$$

$$u_2 = V_s * R_2 / (R_1 + R_2)$$

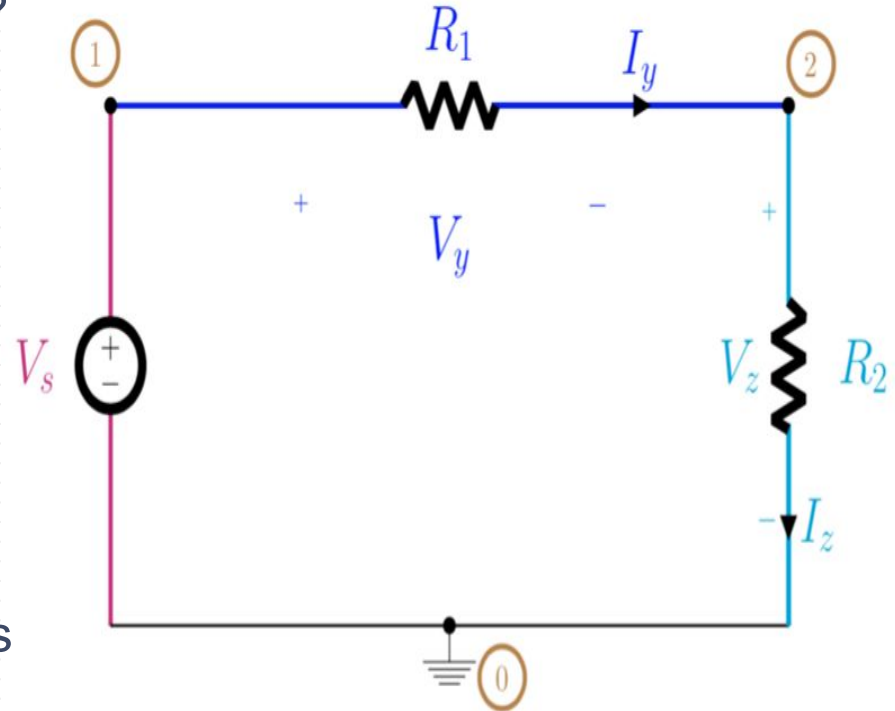
What is the voltage value u_2 if R_1 equals to R_2 ???




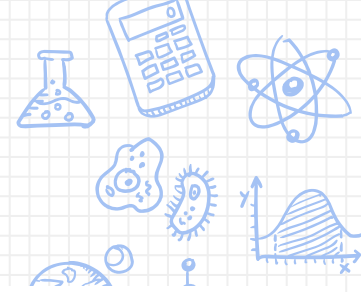

Series and Parallel Resistors

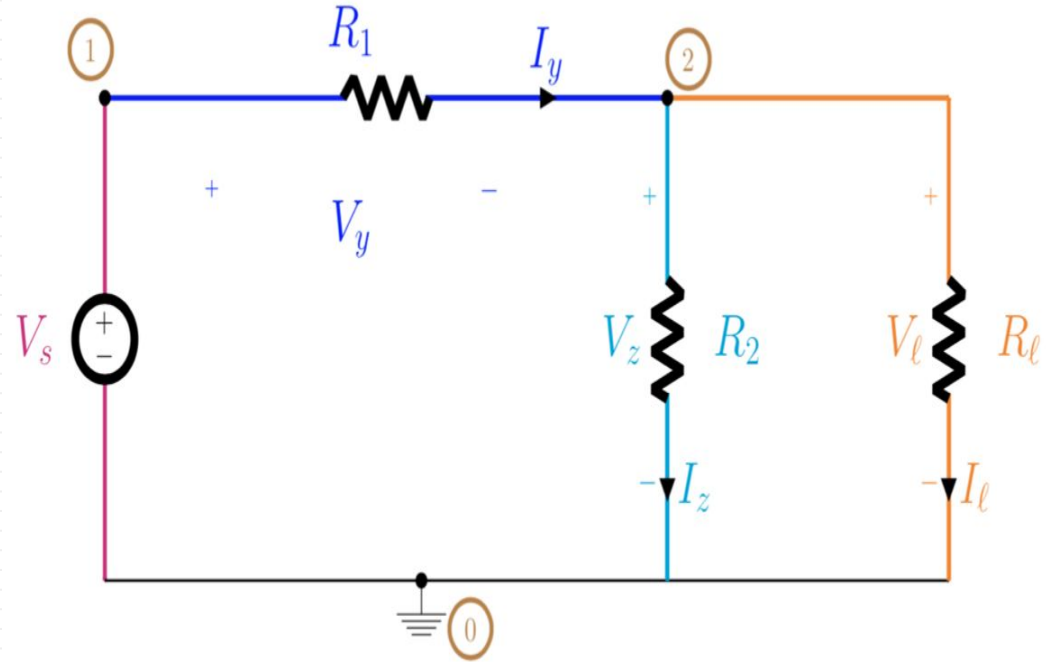- What is the relationship between R_2 and R_l ?
- What about R_l with R_2 and R_l ?



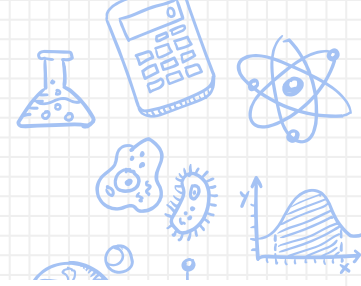


Series and Parallel Resistors

Resistor Equation:

$$R = (\rho * L) / A$$

When in parallel what parameter changes? How does this affect overall resistance, (ie: R_{eq})

What about in series?

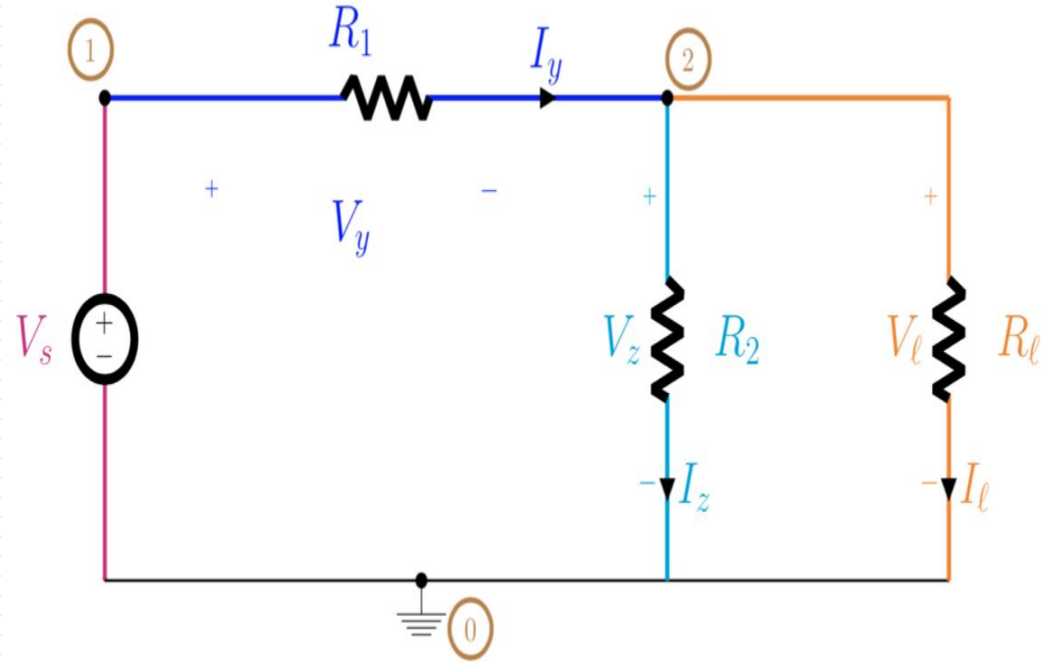

Pointers

- Go through the TinkerCAD tutorial
- Lab Structure:
 - Build in TinkerCAD & Simulate
 - Build on Breadboard and confirm
- Try to debug your circuit by yourself before you ask the TAs
 - However, don't spend too long, after 5 minutes or so queue for help
- Task 3c: MSP acts as single point voltmeter

